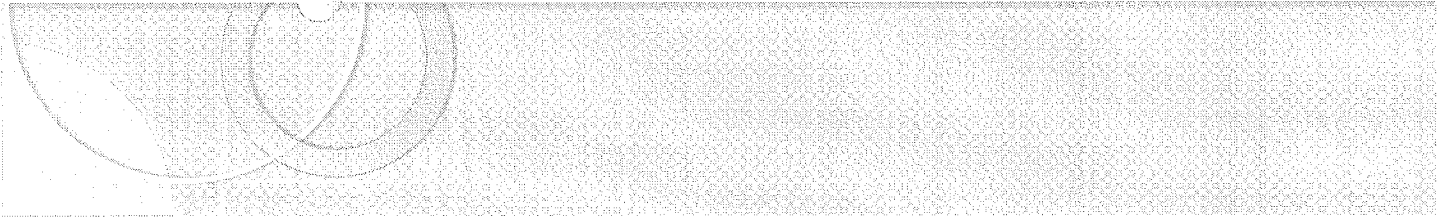


Photomultiplier Tube (PMT) Amplification


Sergio Ribeiro

Alex Maleski



What is a Photomultiplier?

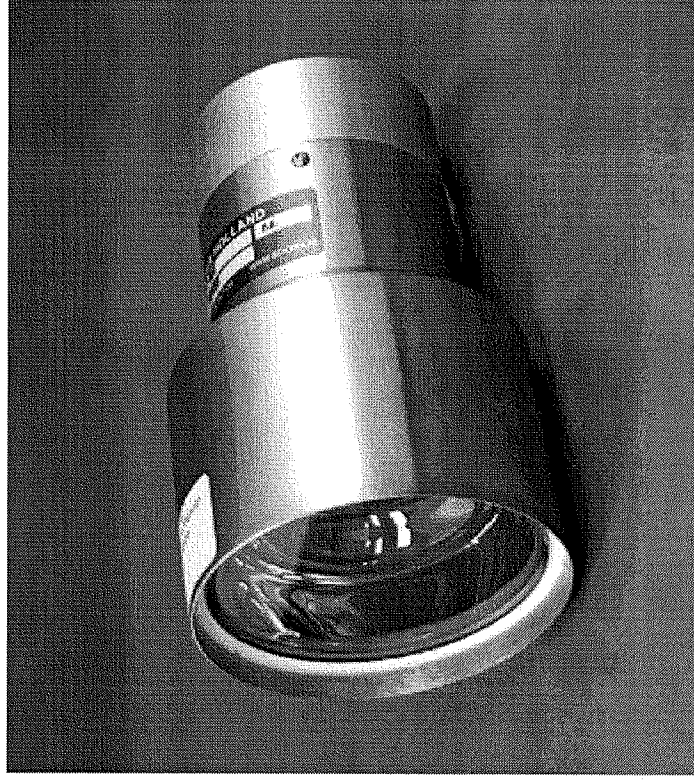
- A photomultiplier is an electronic device used to detect low levels of light



This is a very large PMT. These types are often used in scintillators and various particle detectors.


What is a Photomultiplier?

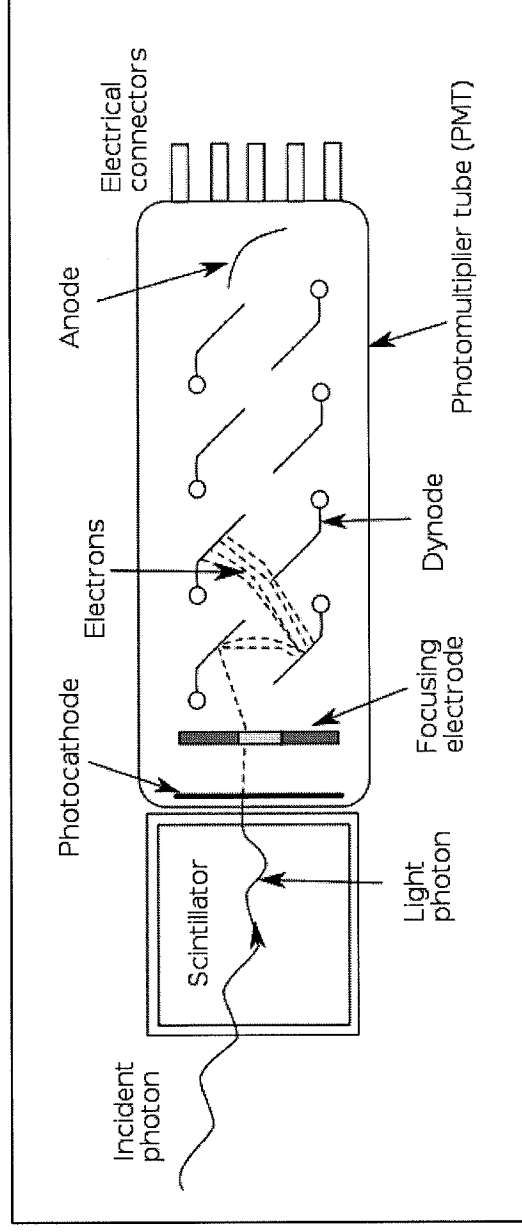- A PMT consists of two basic parts
 - A *photocathode*
 - An *electron multiplier*



What is a Photomultiplier?

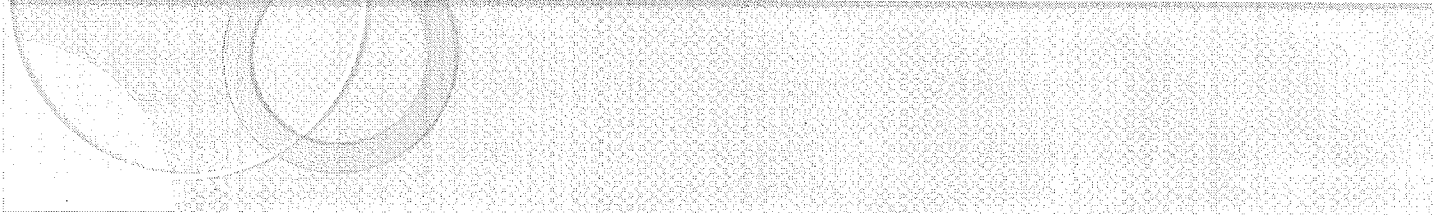- These devices are capable of detecting individual photons
- The electron ejected from the photocathode is “multiplied”
- The cascade of electrons produces a measurable pulse



Why Should We Amplify?

- PMT's produce measurable pulses, however these pulses may be masked by electronic noise from the recording device itself
- If we amplify the signal, we can move the pulses above the noise
 - *Single events and multiple events can be more easily distinguished*
- In addition, amplification prevents electronic noise from being considered as an event

Amplifiers


- There are many different varieties of amplifiers we can consider
- General properties of a suitable amplifier
 - *Low amplifier noise*
 - *High durability*
 - *Fast Response*
 - *Large Bandwidth (slew rate)*
 - *Large Gain*



Operational Amplifiers

- When considering our problem, we decided to use an “operational amplifier” or “op amp” for short.
- Op amps are typically integrated chips and are fairly cheap

Operational Amplifiers

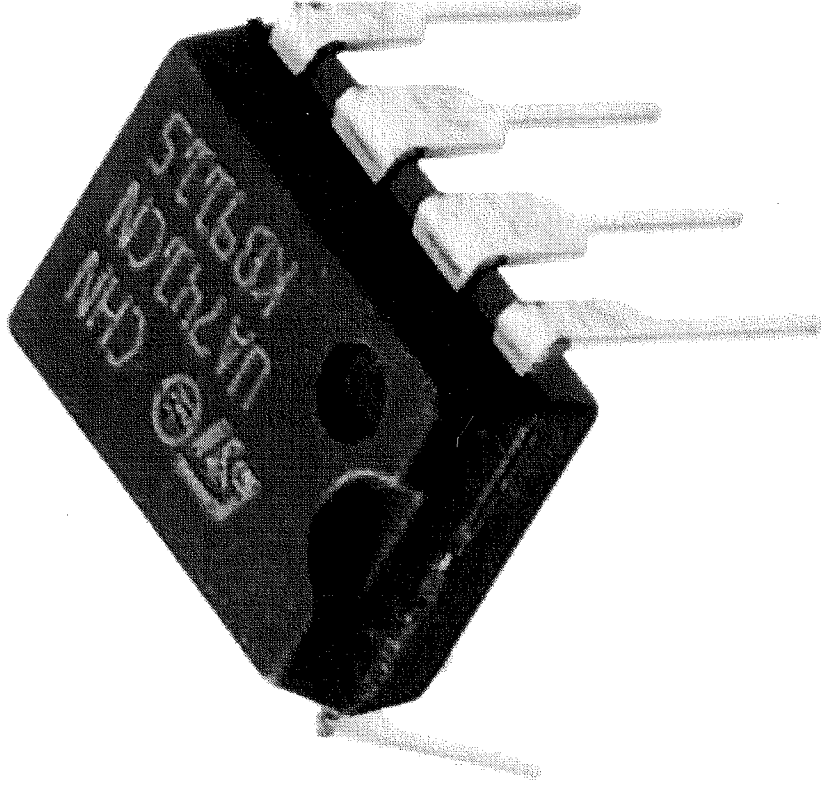

This is the LM741 solid state op amp. This op amp is a very common and very cheap electronic component. This chip is like the Toyota Camry of electronics. Any electronics seller that does not sell this chip is not a real electronics seller.

LM741 Op Amp

- Benefits
 - *The LM741 is a rugged component*
 - *It is very cheap (approximately \$0.50 per chip)*
- Drawbacks
 - *Low slew rate*
 - *Insufficient Bandwidth*


595-THS3202D Fast Op Amp

- Benefits
 - *High slew rate and bandwidth*
 - *Capable of large gain*
- Drawbacks
 - *Small size*
 - *Fragile*
 - *Fairly expensive (\$10.00 per chip)*

Considerations

- When using an amplifier the following components are crucial in determining the success or failure of the module
 - *Power Supply*
 - *Inverting/Non-Inverting*
 - *Current Feedback or Voltage Feedback*
 - *Shielded Cables and Short Cables*
 - *Output/Input Impedances*


Inverting Amplifier

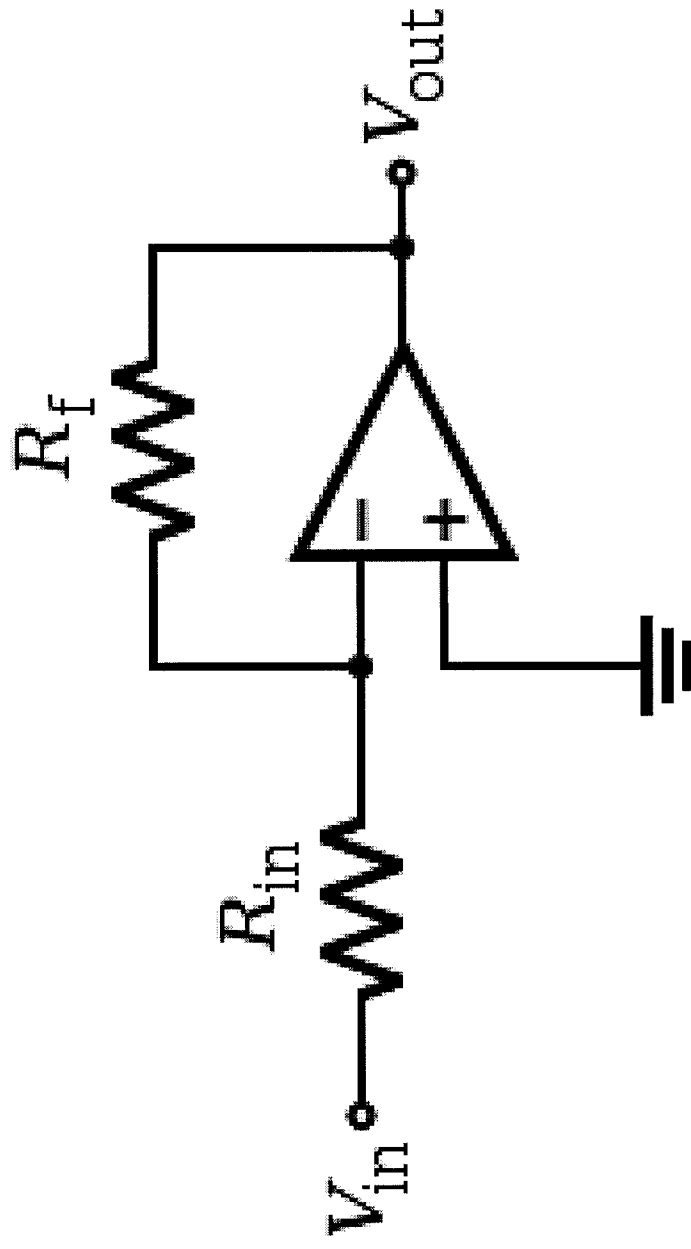

This is an inverting amplifier. An inverting amplifier tends to be more stable in its output than a non-inverting amplifier.

Voltage Feedback Op Amp

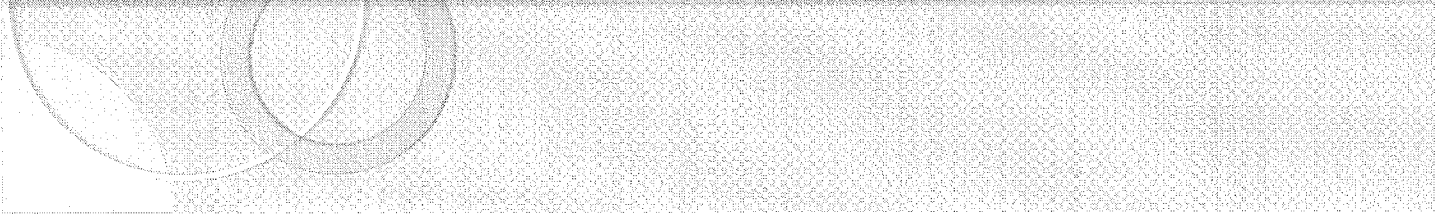- Output voltage is based upon difference of potentials between two terminals
- No minimum resistance is required to stabilize the output
- The LM741 op amp is a voltage feedback amplifier (VFA)



Current Feedback Op Amp



- Output voltage is based upon a difference in currents between the input terminals
- A minimum resistance on the input terminals is required to stabilize the output
- The 595-THS3202D is a Current Feedback Amplifier (CFA)




Drawbacks of a CFA

- If no resistor is placed in series with input terminal, the amplifier may begin to oscillate
- This will cause the amplifier to oscillate at its own frequency which will swamp out the original signal

Circuit Design

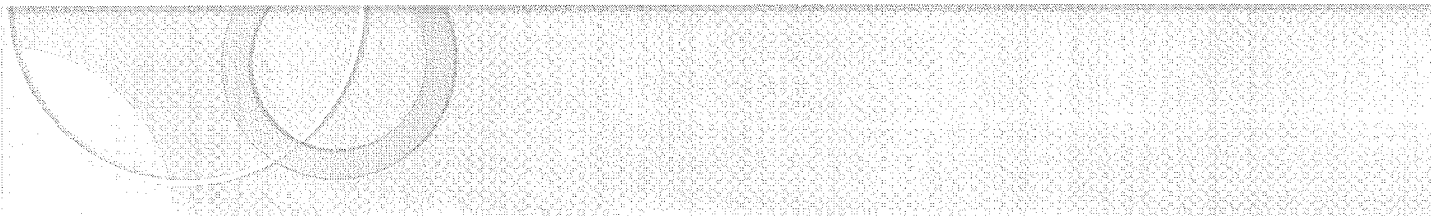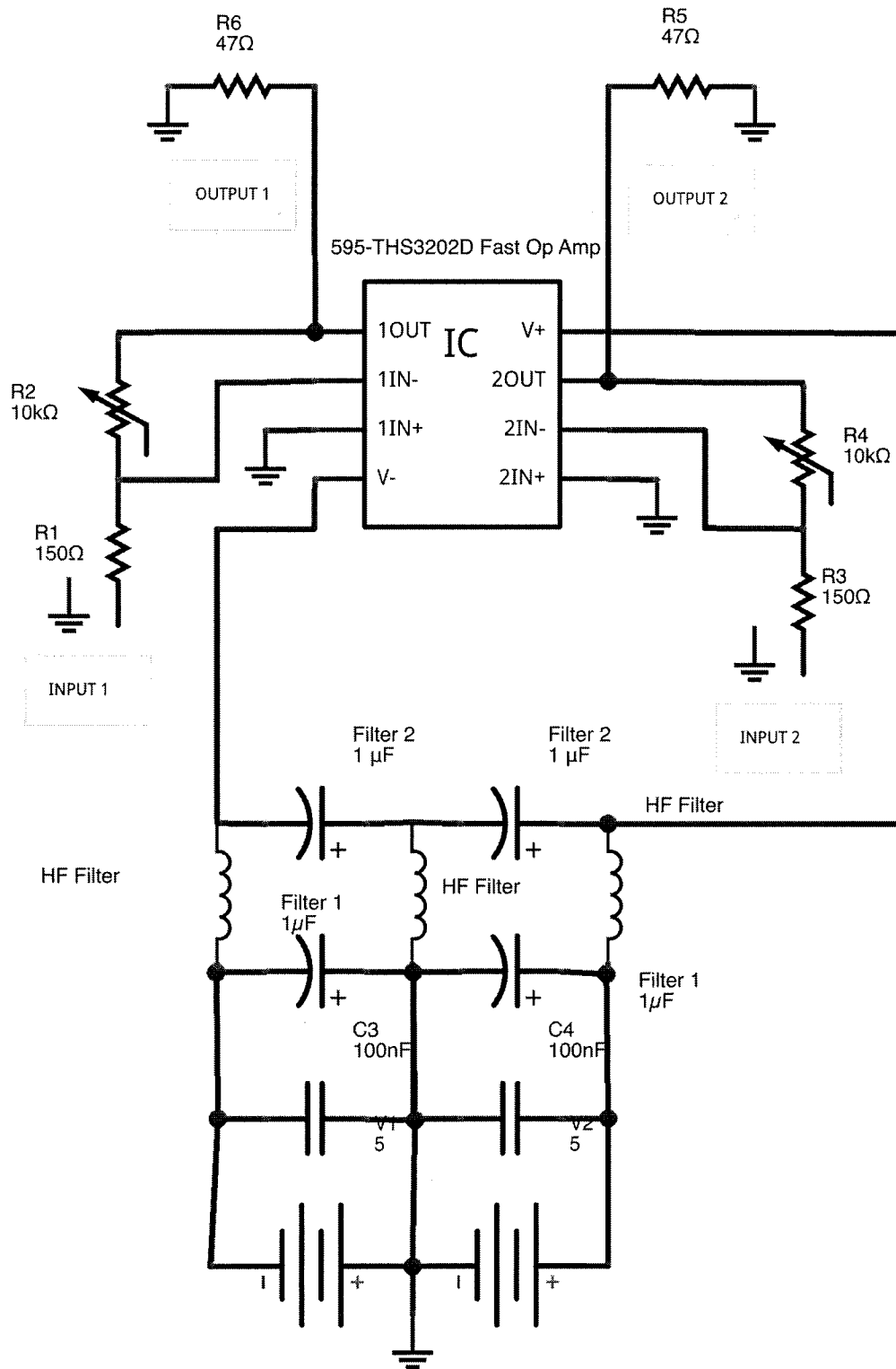


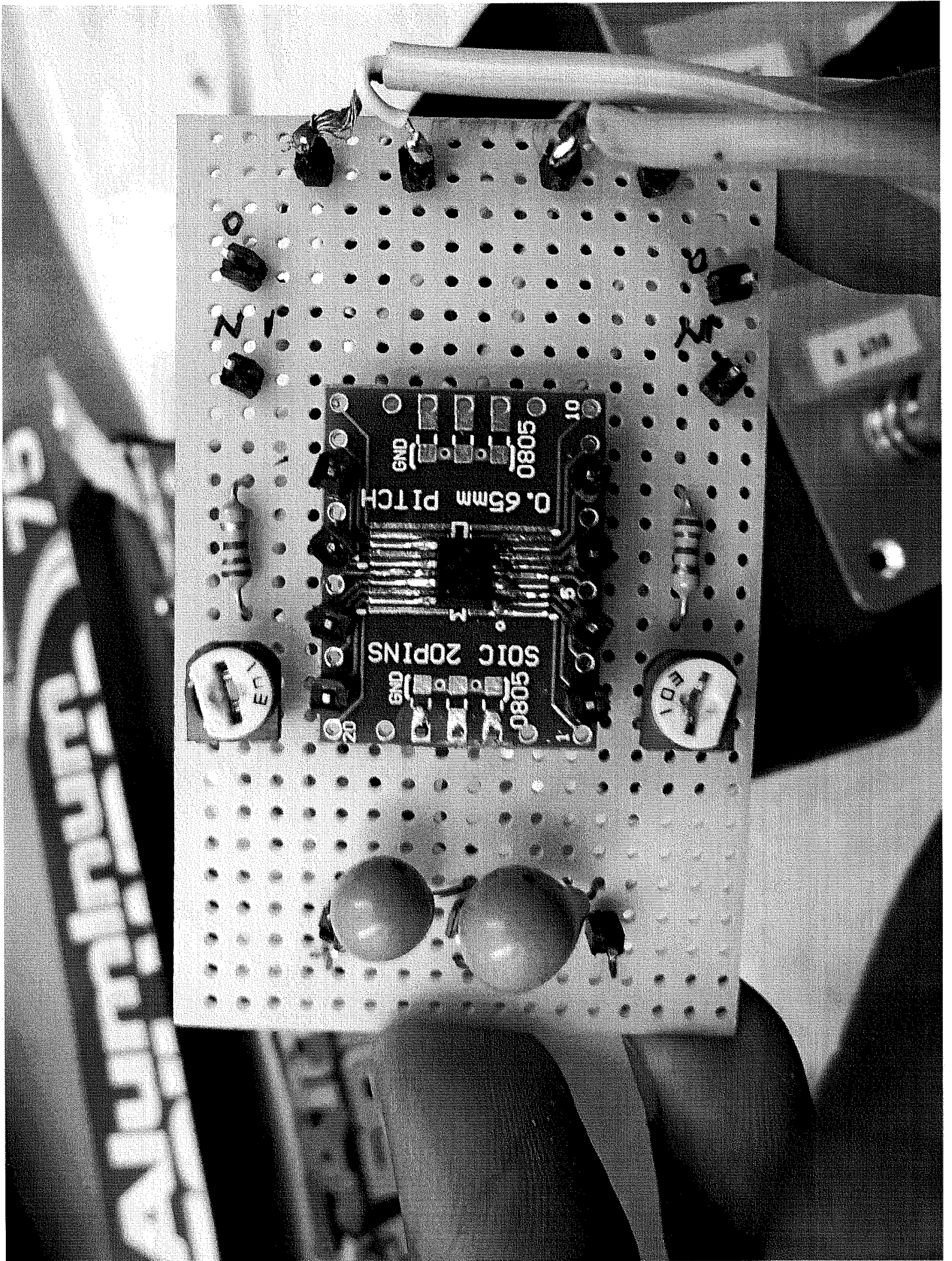



5085 SOIC 20PINS
0.65mm PITCH
5085

100V

100V

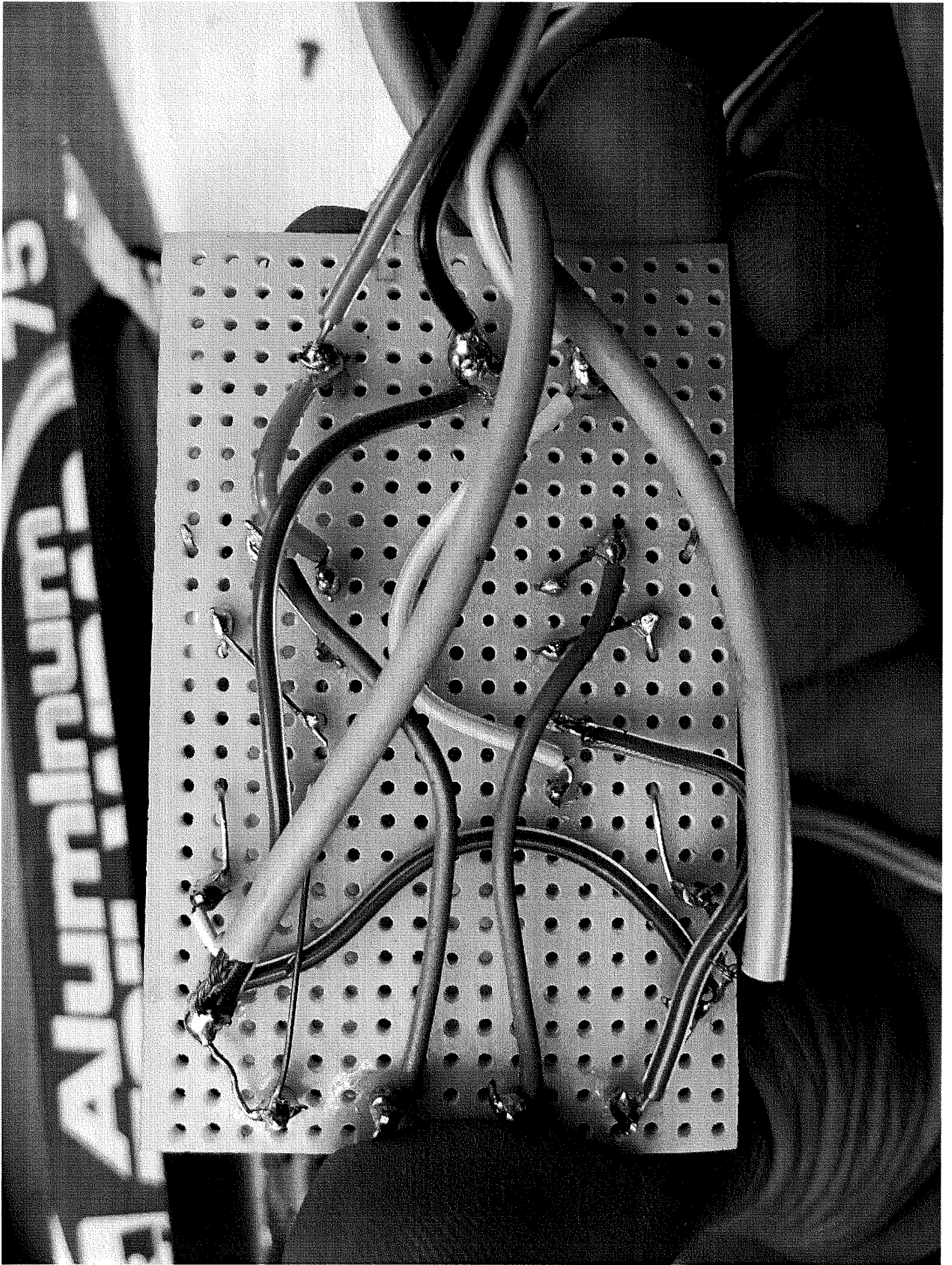

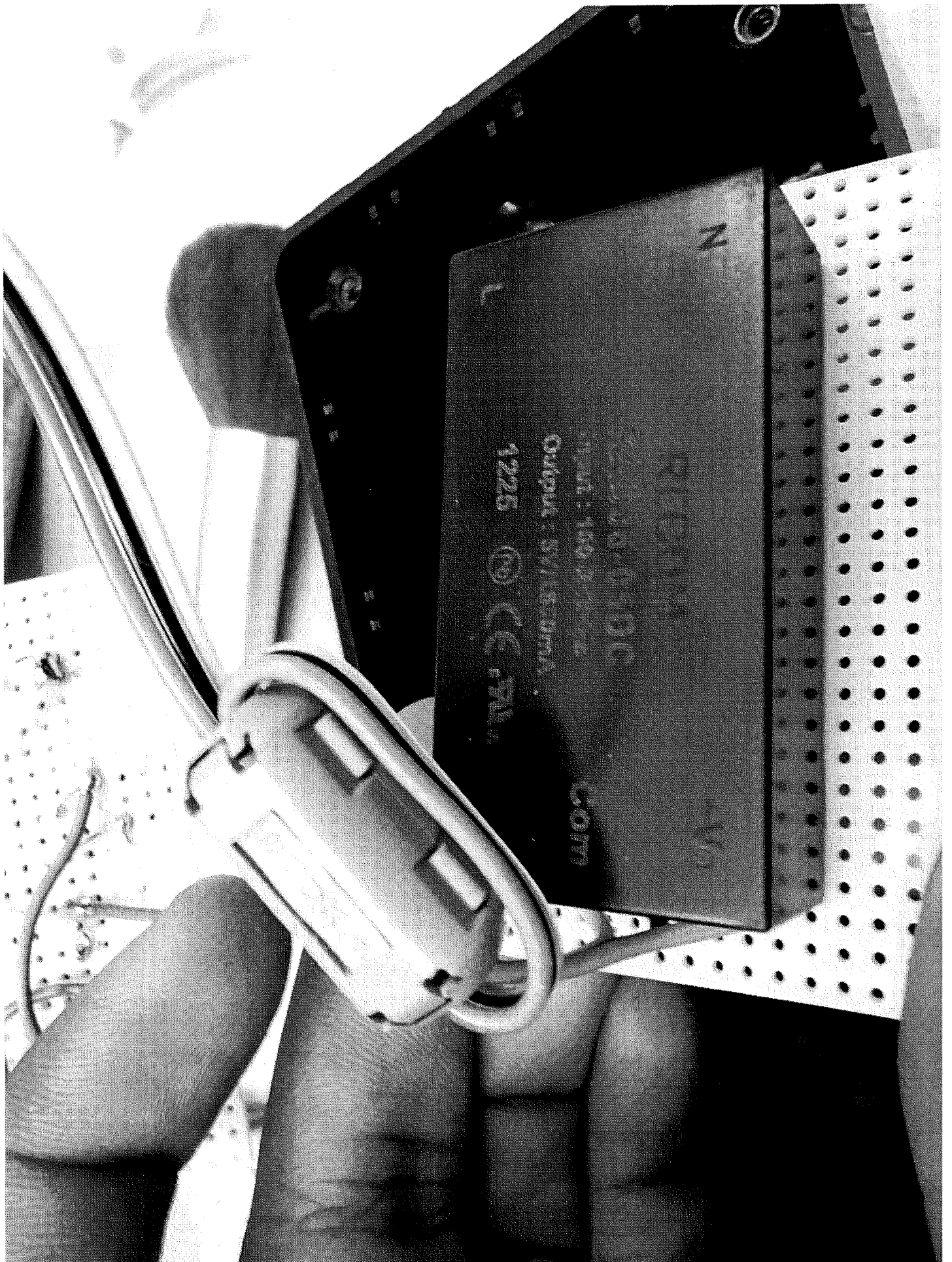

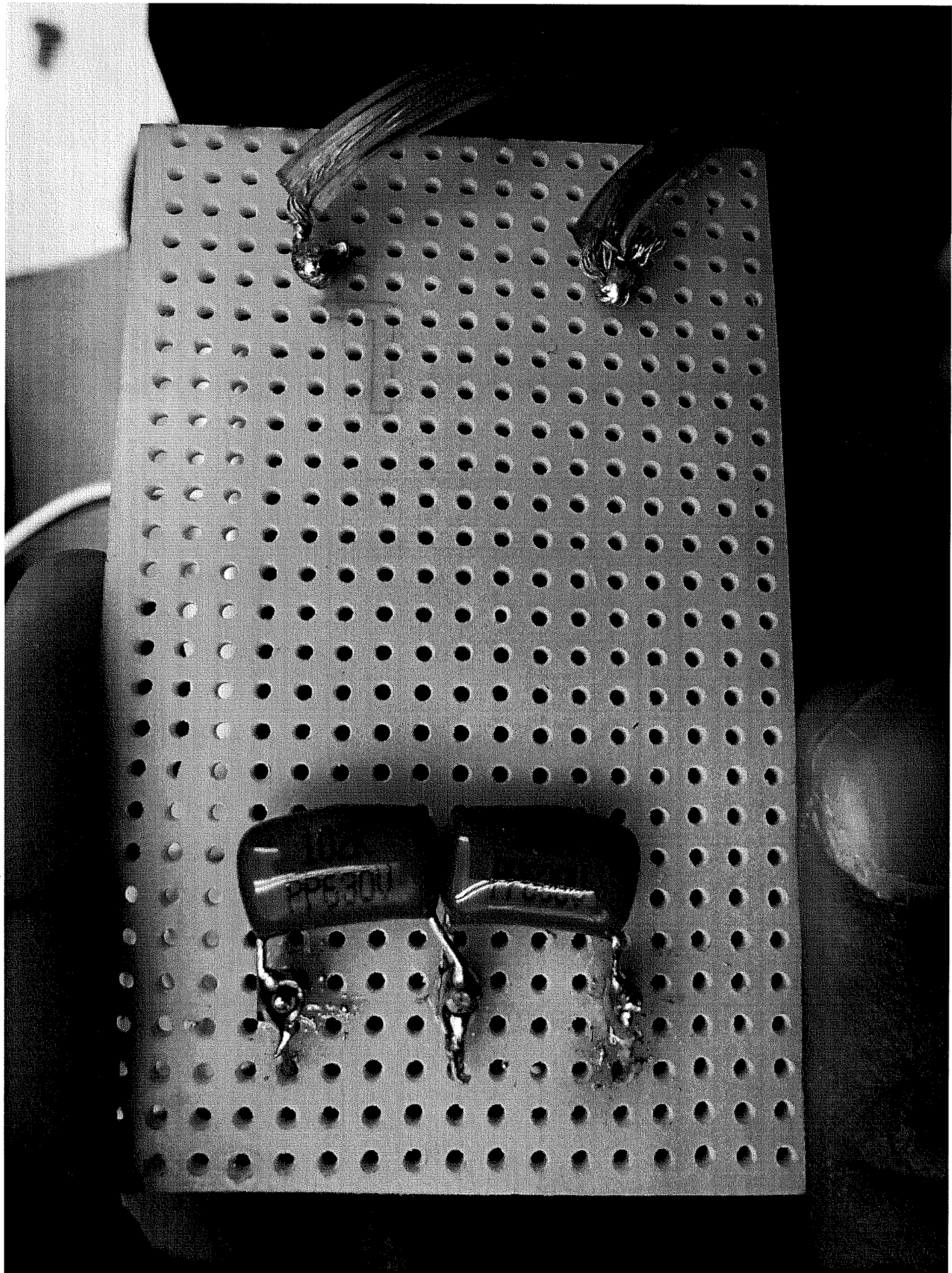





Amplifier Tests

- The amplifier was tested with a frequency sweep from 0 to 3 MHz with a sinusoidal waveform
- In addition the amplifier was tested with an Avtech AV-1030-C pulse generator


Gain (dB) vs. Frequency (Hz)

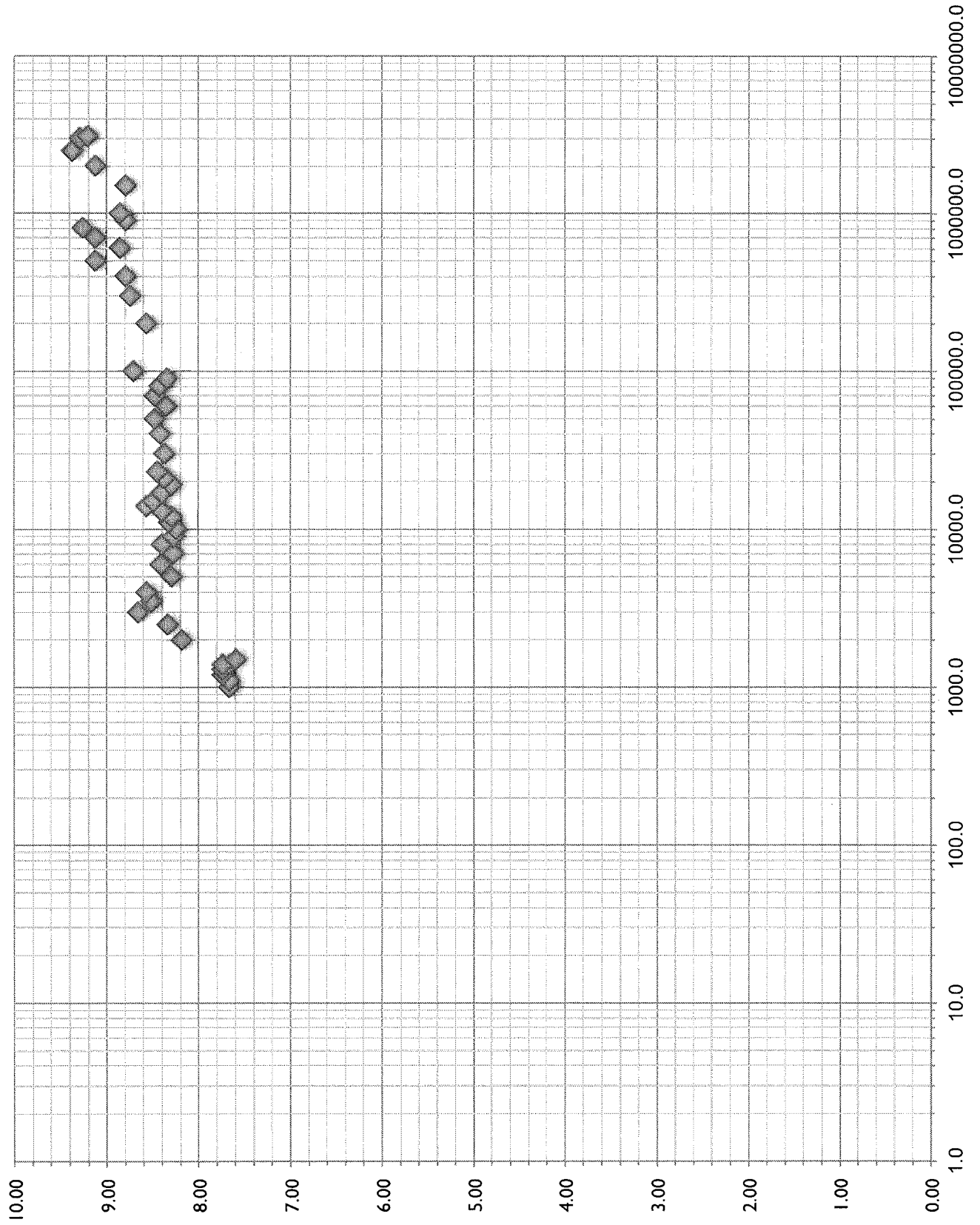


15 nanosecond pulse

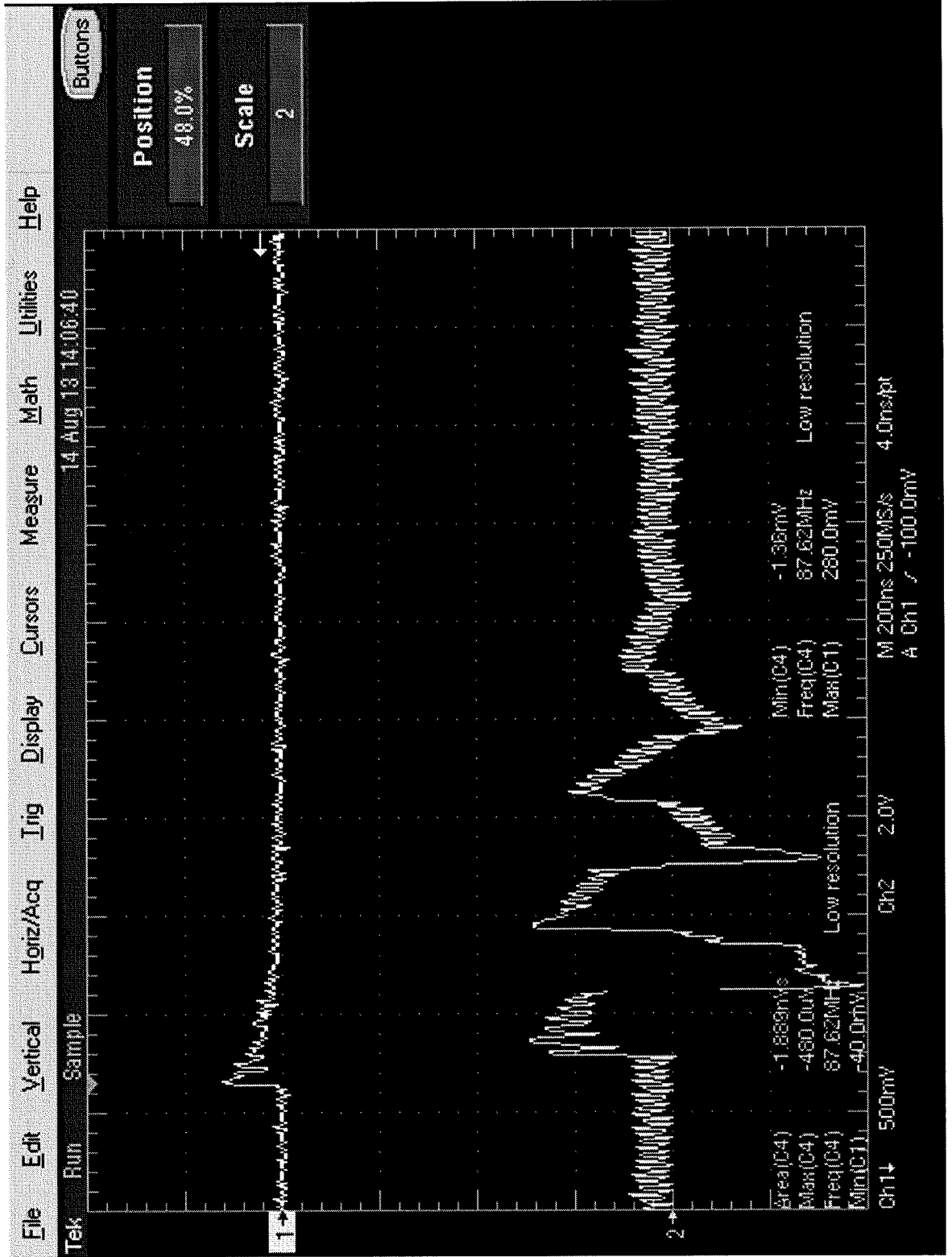


100 nanosecond pulse

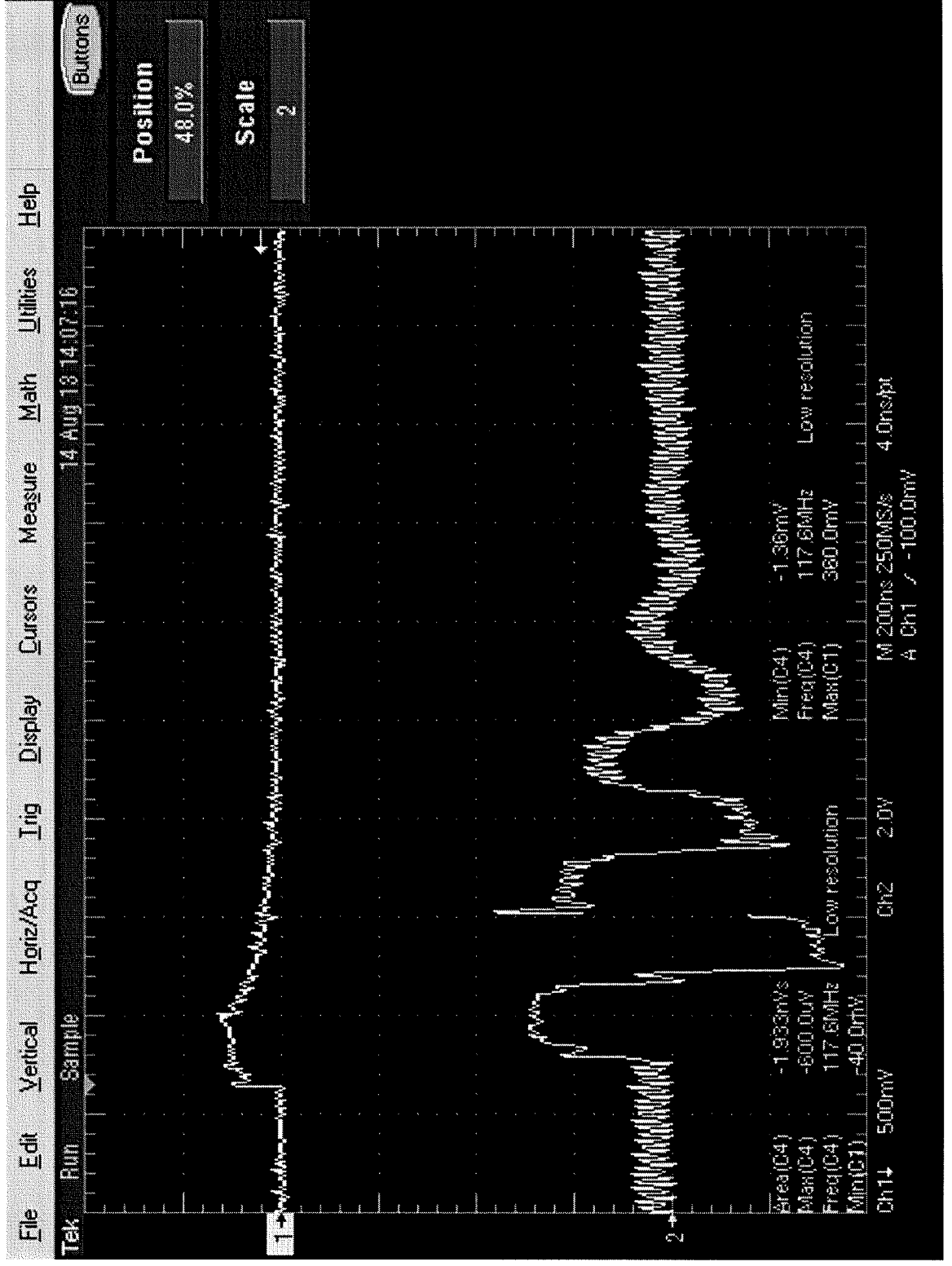


1 microsecond pulse

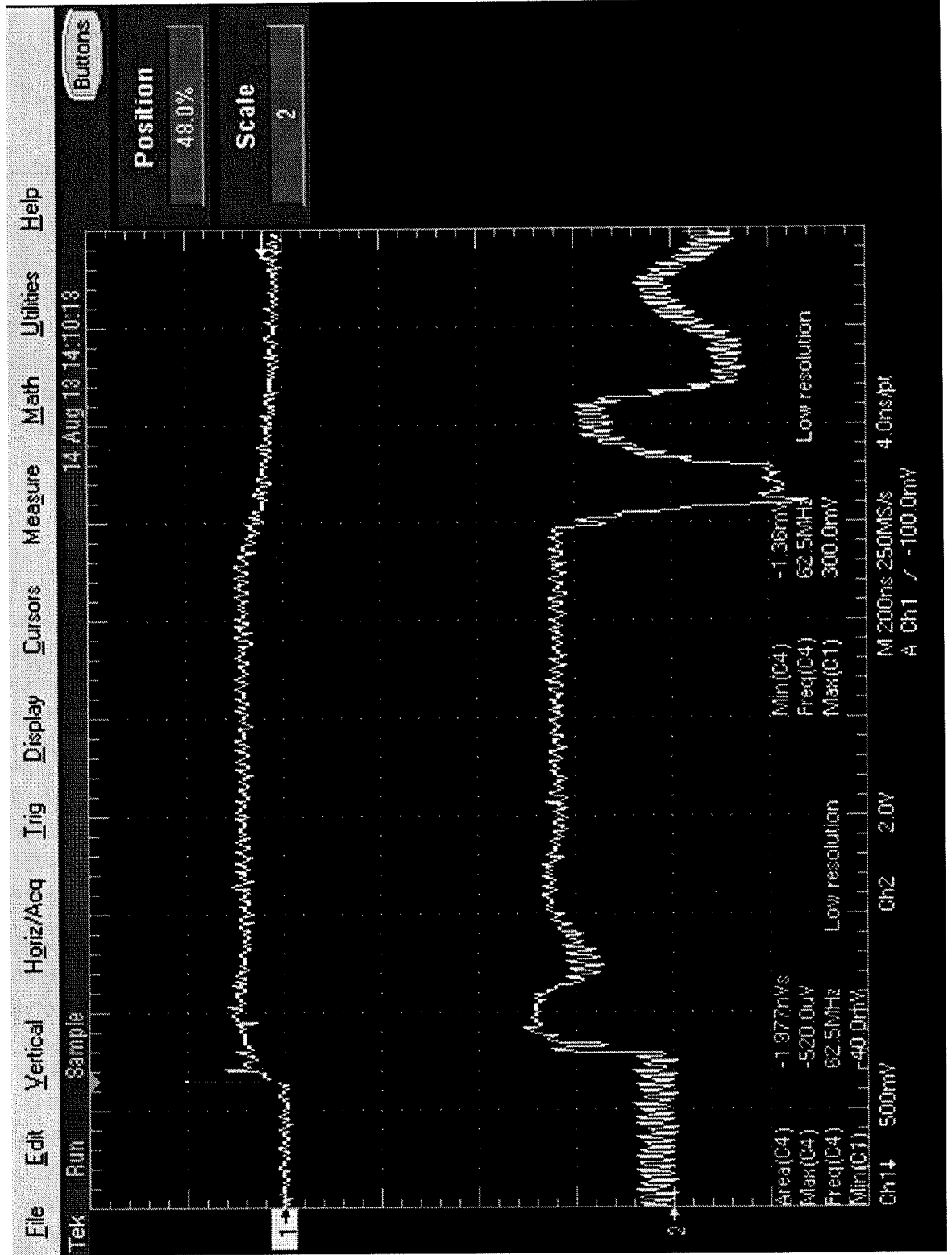

10 microsecond pulse

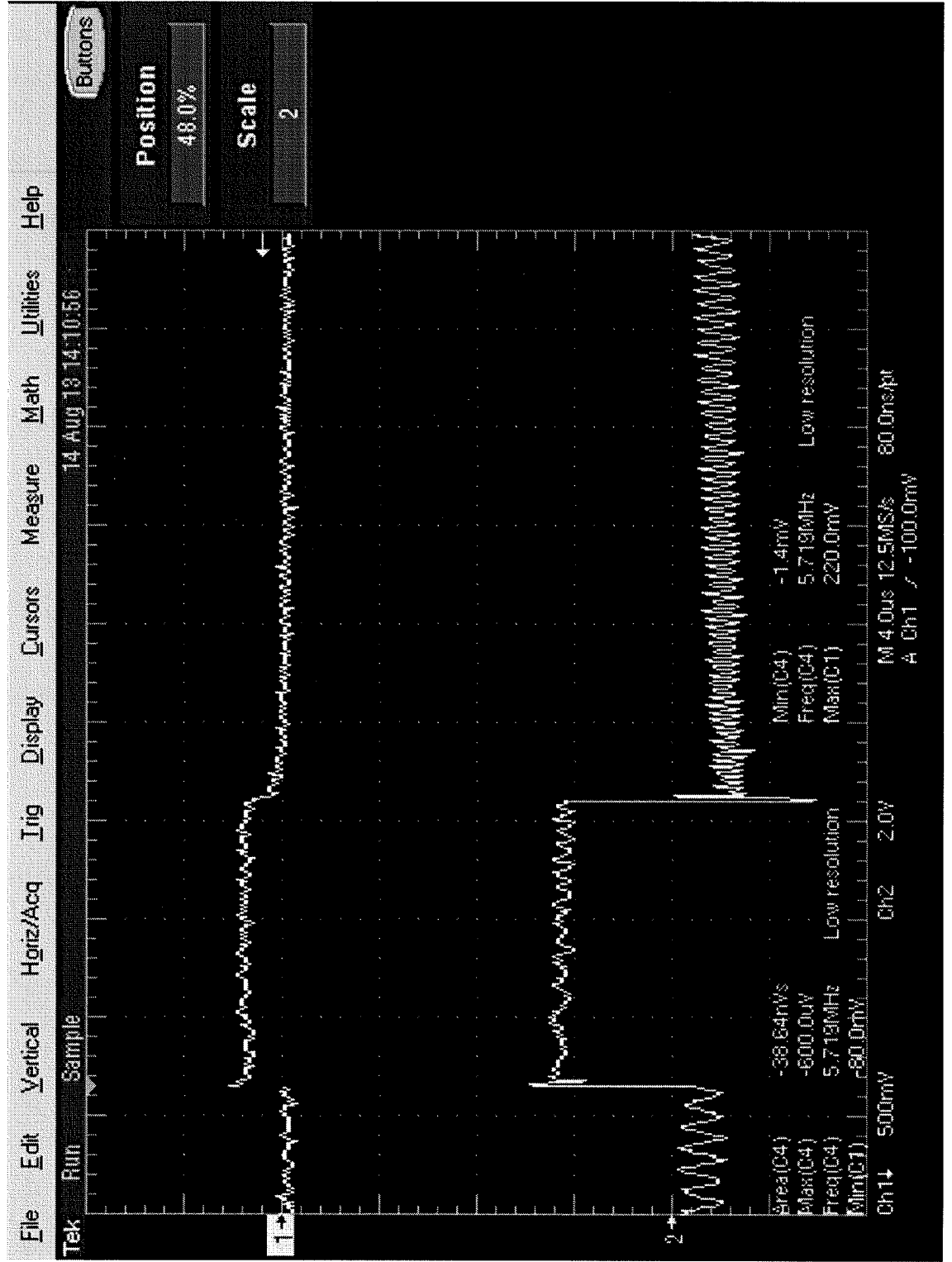

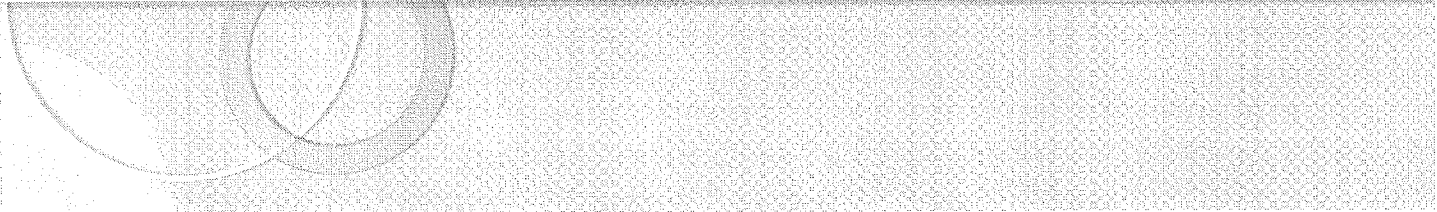

Conclusion

- From our frequency sweep tests and our pulse generator tests, we have shown that the 595-THS3202D fast op amp is adequate for the amplification of a PMT signal
- This amplifier is adequate for many nuclear physics experiments

Questions?

