

PMT Progress



SERGIO RIBEIRO
ALEX MALESKI

Amplifier Noise



- A constant 28 MHz signal is present in the output
- Power supply is suspected
 - Due to the fact that the power supply is a switching power supply
 - It can be modified to produce less noise however

Switching Power Supply




- A switching power supply is typically used in devices that need compactness
 - Typically found in cellphone chargers
 - Found in computer power supplies
 - Use very high frequency AC

Switching Power Supply



- A switching power supply is compact based on the skin effect
- At high frequencies, electricity conducts only on the surface of a conductor
- Litz wire is very thin wire meant for conducting at high frequencies
- As a result the high frequency allows for smaller more compact power supplies

Switching Power Supply

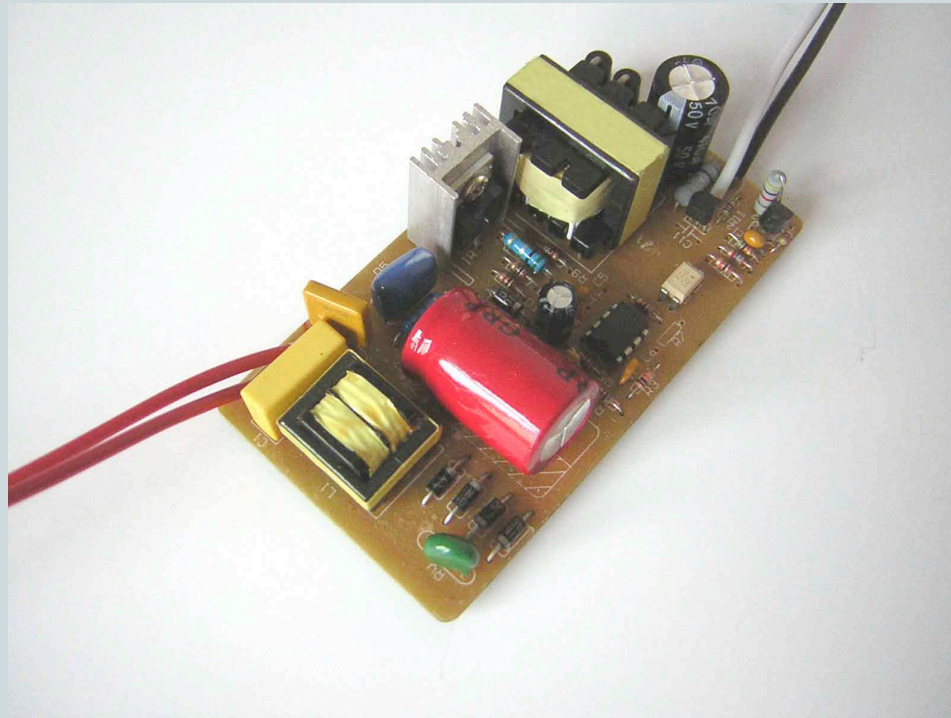

Power Supply Solution



- Capacitors to bypass high frequency noise
- Inductors to create impedance at high frequencies
- RC filters or RL filters
- Alternatively we can build our own power supply
 - Simple two battery supply
 - Power supply ripple would be very small

Goals



- Eventually we would place our amplifier in a box where you can plug a BNC connector into the input and a BNC connector into the output.
- The amplifier chip actually contains two amplifiers, so later this box could amplify two incoming signals.